

```
-- CS214 Practical 5 Memo
-- authors: MJ Booyesen and RD Beyers
-- updated on 16 April 2015
```

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
use ieee.numeric_std.all;
LIBRARY altera;
use altera.altera_primitives_components.all;
```

```
ENTITY DE0 IS
    PORT
```

```
(
    CLOCK_50 : IN STD_LOGIC; -- 50MHz in-circuit clock
    LEDG : OUT STD_LOGIC_VECTOR(9 DOWNTO 0); -- the 10 green LEDs on
the DE0 board
    SW : IN STD_LOGIC_VECTOR(9 DOWNTO 0); -- the 10 switches on the
DE0 board
    BUTTON : IN STD_LOGIC_VECTOR(0 TO 2); -- the 3 buttons on the
DE0 board
    HEX0_D : INOUT STD_LOGIC_VECTOR(0 TO 6); -- the LEDs of the
7-segment display (right)
    HEX1_D : INOUT STD_LOGIC_VECTOR(0 TO 6); -- the LEDs of the
7-segment display
    HEX2_D : INOUT STD_LOGIC_VECTOR(0 TO 6); -- the LEDs of the
7-segment display
    HEX3_D : INOUT STD_LOGIC_VECTOR(0 TO 6); -- the LEDs of the
7-segment display (left)
    FL_BYTE_N : IN STD_LOGIC;
    FL_CE_N : IN STD_LOGIC;
    FL_OE_N : IN STD_LOGIC;
    FL_RST_N : IN STD_LOGIC;
    FL_RY : IN STD_LOGIC;
    FL_WE_N : IN STD_LOGIC;
    FL_WP_N : IN STD_LOGIC;
    FL_DQ15_AM1 : IN STD_LOGIC;
    PS2_KBCLK : IN STD_LOGIC;
    PS2_KBDAT : IN STD_LOGIC;
    PS2_MSCLK : IN STD_LOGIC;
    PS2_MS DAT : IN STD_LOGIC;
    UART_RXD : IN STD_LOGIC;
    UART_TXD : IN STD_LOGIC;
    UART_RTS : IN STD_LOGIC;
    UART_CTS : IN STD_LOGIC;
    SD_CLK : IN STD_LOGIC;
    SD_CMD : IN STD_LOGIC;
    SD_DAT0 : IN STD_LOGIC;
    SD_DAT3 : IN STD_LOGIC;
    SD_WP_N : IN STD_LOGIC;
    LCD_RW : IN STD_LOGIC;
    LCD_RS : IN STD_LOGIC;
    LCD_EN : IN STD_LOGIC;
    LCD_BLON : IN STD_LOGIC;
    VGA_HS : IN STD_LOGIC;
    VGA_VS : IN STD_LOGIC;
    HEX0_DP : IN STD_LOGIC;
    HEX1_DP : IN STD_LOGIC;
    HEX2_DP : IN STD_LOGIC;
    HEX3_DP : IN STD_LOGIC;
    DRAM_CAS_N : IN STD_LOGIC;
    DRAM_CS_N : IN STD_LOGIC;
    DRAM_CLK : IN STD_LOGIC;
    DRAM_CKE : IN STD_LOGIC;
    DRAM_BA_0 : IN STD_LOGIC;
    DRAM_BA_1 : IN STD_LOGIC;
    DRAM_LDQM : IN STD_LOGIC;
    DRAM_UDQM : IN STD_LOGIC;
```

```

                                DE0.txt
DRAM_RAS_N : IN STD_LOGIC;
DRAM_WE_N : IN STD_LOGIC;
CLOCK_50_2 : IN STD_LOGIC;
FL_ADDR : IN STD_LOGIC_VECTOR(0 TO 21);
FL_DQ : IN STD_LOGIC_VECTOR(0 TO 14);
GPIO0_D : INOUT STD_LOGIC_VECTOR(0 TO 31);
GPIO0_CLKIN : IN STD_LOGIC_VECTOR(0 TO 1);
GPIO0_CLKOUT : IN STD_LOGIC_VECTOR(0 TO 1);
GPIO1_CLKIN : IN STD_LOGIC_VECTOR(0 TO 1);
GPIO1_CLKOUT : IN STD_LOGIC_VECTOR(0 TO 1);
GPIO1_D : IN STD_LOGIC_VECTOR(0 TO 31);
LCD_DATA : IN STD_LOGIC_VECTOR(0 TO 7);
VGA_G : IN STD_LOGIC_VECTOR(0 TO 3);
VGA_R : IN STD_LOGIC_VECTOR(0 TO 3);
VGA_B : IN STD_LOGIC_VECTOR(0 TO 3);
DRAM_DQ : IN STD_LOGIC_VECTOR(0 TO 15);
DRAM_ADDR : IN STD_LOGIC_VECTOR(0 TO 12)
);

END DE0;

ARCHITECTURE structure OF DE0 IS
    SIGNAL SUB_CLK : STD_LOGIC;
    SIGNAL Counter : INTEGER := 0;
BEGIN
    -- xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx --
    -- Question 1
    -- xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx --
    LEDG(0) <= NOT button(0);

    -- xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx --
    -- Question 2
    -- xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx --
    LEDG(1) <= button(1)XOR button(0);

    -- xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx --
    -- Question 3
    -- xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx --
    u1: dff PORT MAP (d => NOT Button (0), clk => NOT Button (1),
                    clrn => Button (2), prn=> '1', q => LEDG(2));

    -- xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx --
    -- Question 4
    -- xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx --
    WITH SW(3 DOWNT0 0) SELECT
        HEX0_D <= NOT "1111110" WHEN "0000",
                NOT "0110000" WHEN "0001",
                "0010010" when "0010",
                "0000110" when "0011",
                "1001100" when "0100",
                "0100100" when "0101",
                "0100000" when "0110",
                "0001111" when "0111",
                "0000000" when "1000",
                "0000100" when "1001",
                "0001000" when "1010",
                "1100000" when "1011",
                "0110001" when "1100",
                "1000010" when "1101",
                "0110000" when "1110",
                "0111000" when "1111";

    -- xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx --
    -- Question 5
    -- xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx --
    PROCESS (CLOCK_50)
        VARIABLE SUB_CLK_CNT : INTEGER RANGE 0 TO 25000000;
    BEGIN
        IF CLOCK_50'EVENT AND CLOCK_50 = '1' THEN

```

```

DE0.txt
SUB_CLK_CNT := SUB_CLK_CNT + 1;
IF SUB_CLK_CNT = 25000000 THEN
    SUB_CLK_CNT := 0;
    SUB_CLK <= NOT SUB_CLK;
END IF;
END IF;
END PROCESS;
LEDG(3)<= SUB_CLK;

-- xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx --
-- Question 6
-- xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx --
PROCESS (SUB_CLK)
BEGIN
    IF SUB_CLK'EVENT AND SUB_CLK = '1' THEN
        IF SW(9) = '0' THEN
            Counter <= Counter + 1;
            IF Counter >= 99 THEN Counter <= 0; END IF;
        ELSE
            Counter <= Counter - 1;
            IF Counter <= 0 THEN Counter <= 99; END IF;
        END IF;
    END IF;
END PROCESS;
WITH Counter REM 10 SELECT
    HEX2_D <= NOT "1111110" WHEN 0,
    NOT "0110000" WHEN 1,
    "0010010" when 2,
    "0000110" when 3,
    "1001100" when 4,
    "0100100" when 5,
    "0100000" when 6,
    "0001111" when 7,
    "0000000" when 8,
    "0000100" when 9,
    "0110000" when OTHERS;
WITH (Counter/10) SELECT
    HEX3_D <= NOT "1111110" WHEN 0,
    NOT "0110000" WHEN 1,
    "0010010" when 2,
    "0000110" when 3,
    "1001100" when 4,
    "0100100" when 5,
    "0100000" when 6,
    "0001111" when 7,
    "0000000" when 8,
    "0000100" when 9,
    "0110000" when OTHERS;

END structure;

```